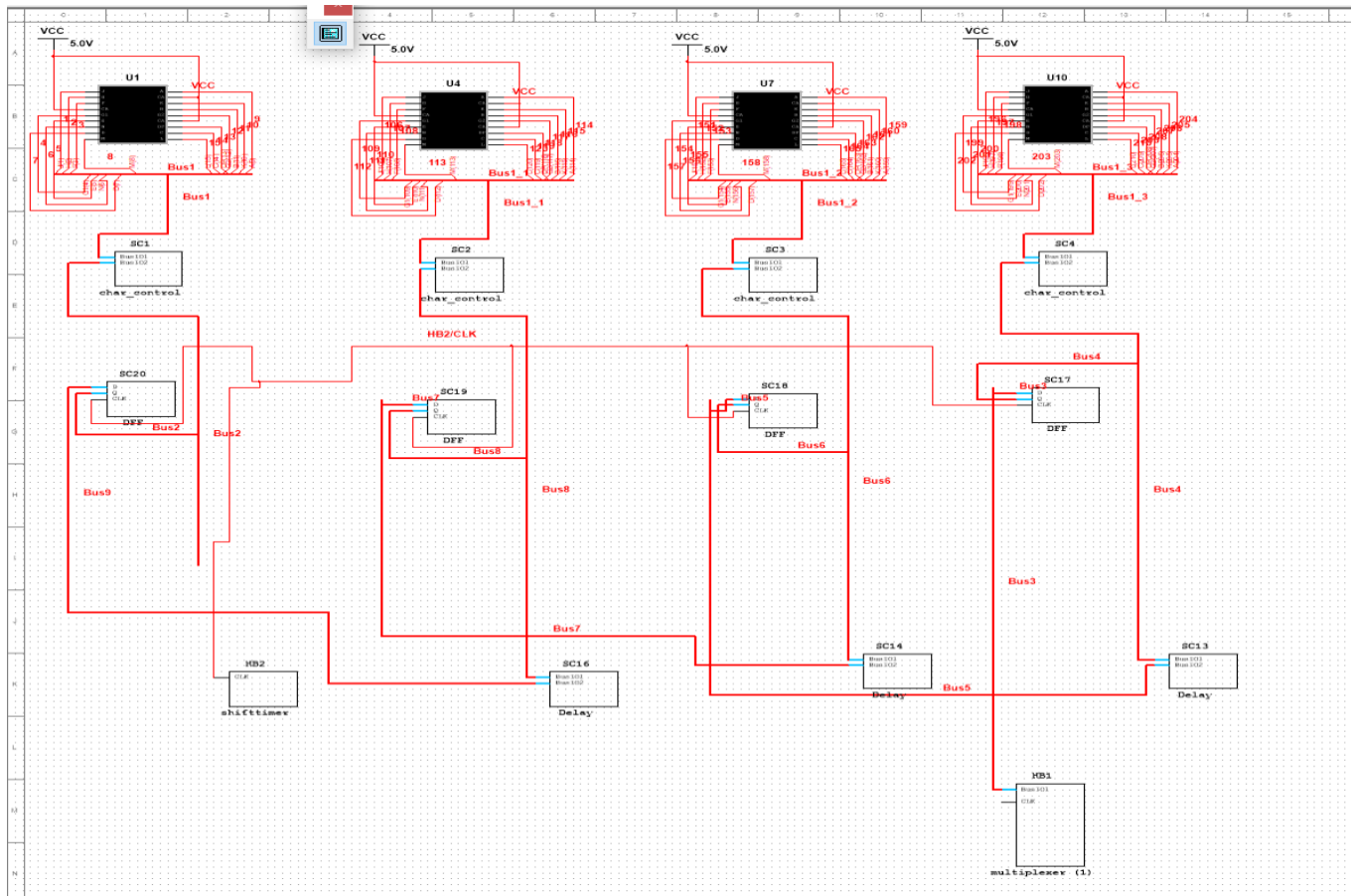


ELECTRONIC DEVICES AND CIRCUITS LAB

Dynamic Ads Display


14th May 2020

Main Circuit: -




Sub-Circuits: -


Character Control Circuit: -

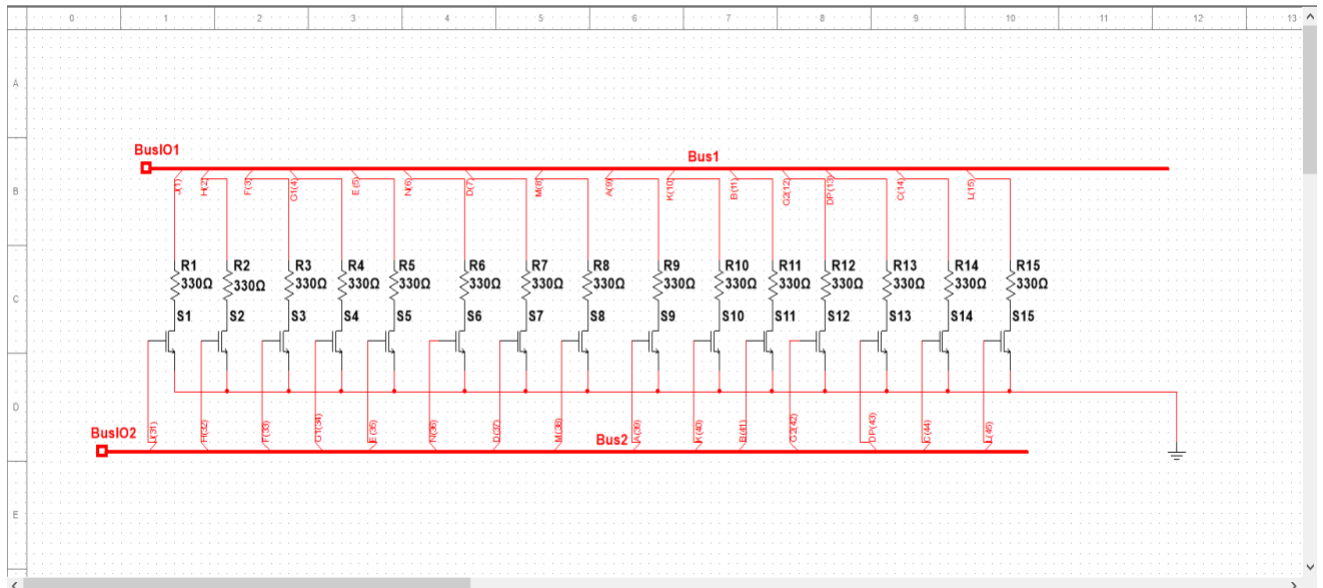


All Multiplexers Main Circuit: -

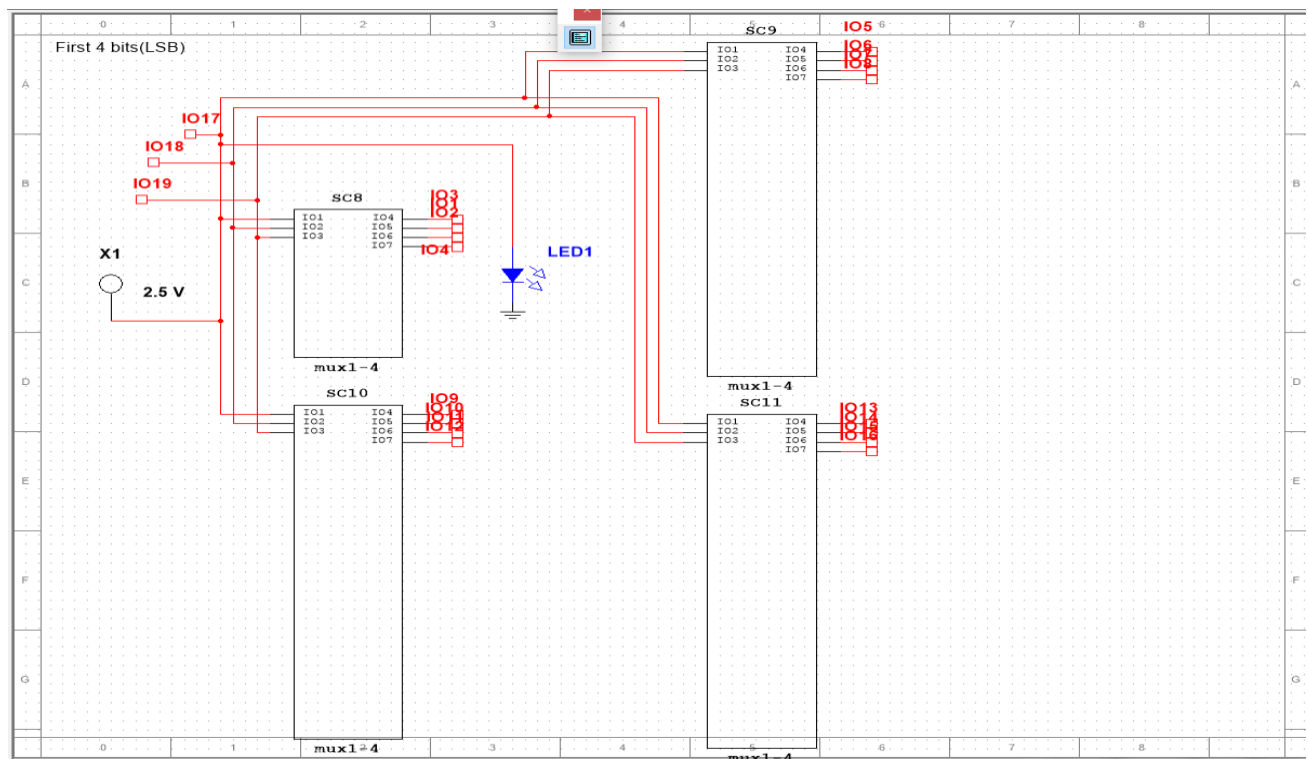


4x1 Multiplexer Circuit: -

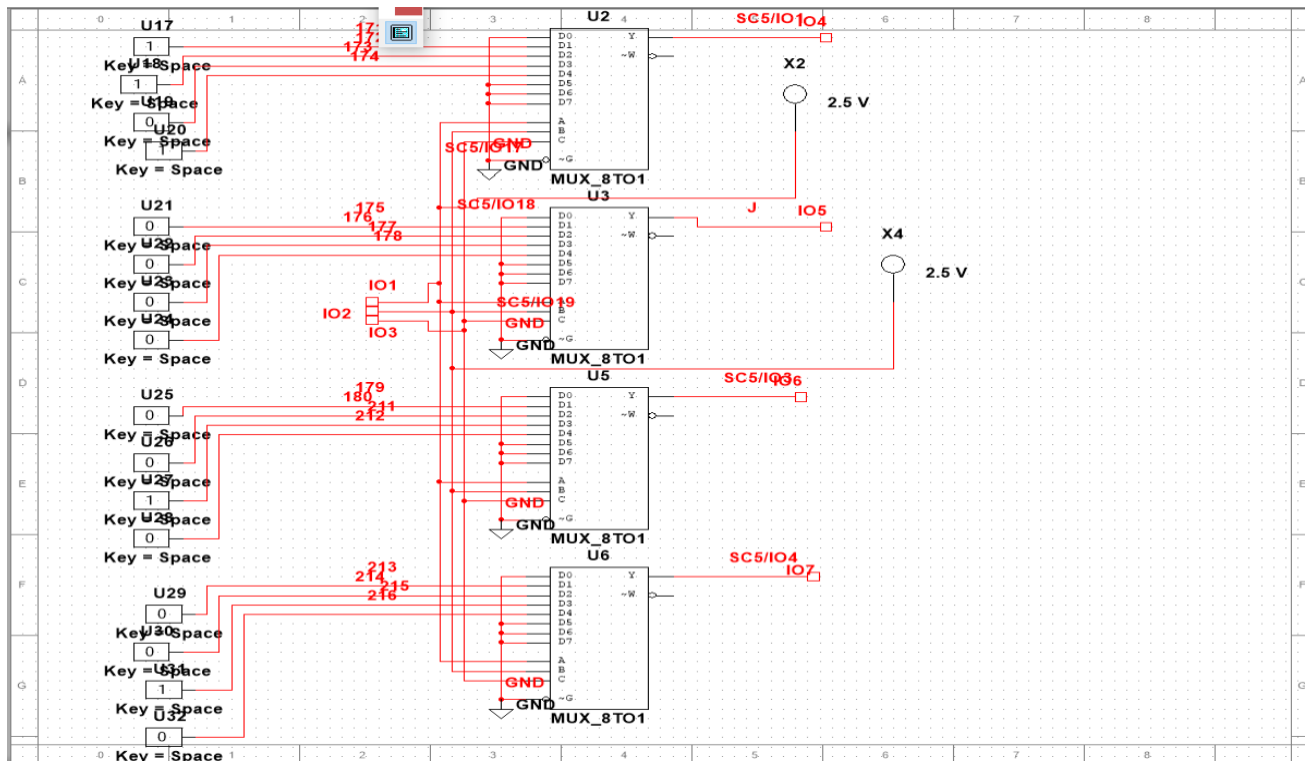


Counter Main Circuit: -

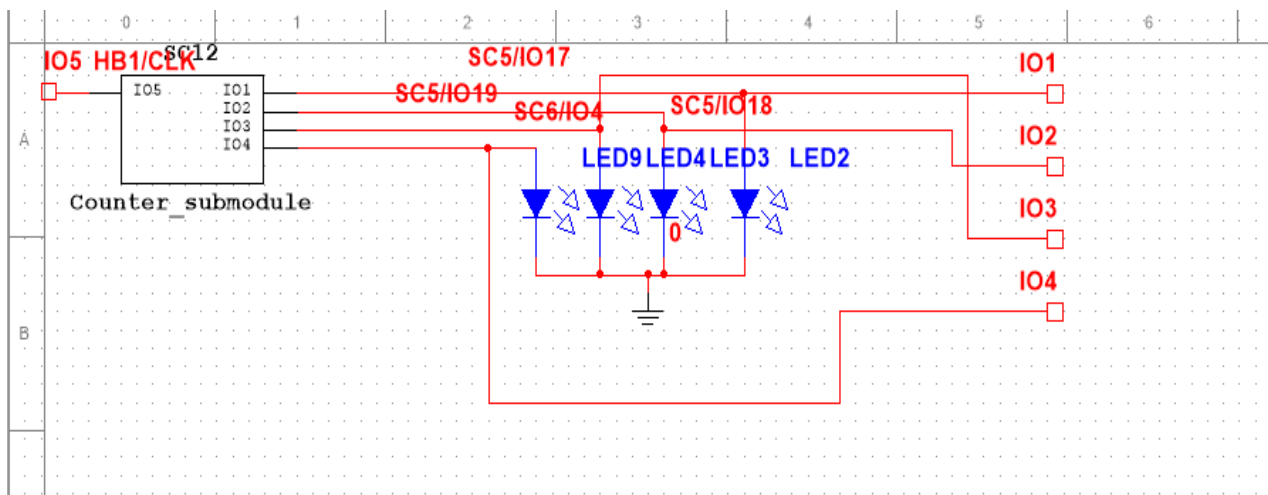


Counter Sub-Module: -

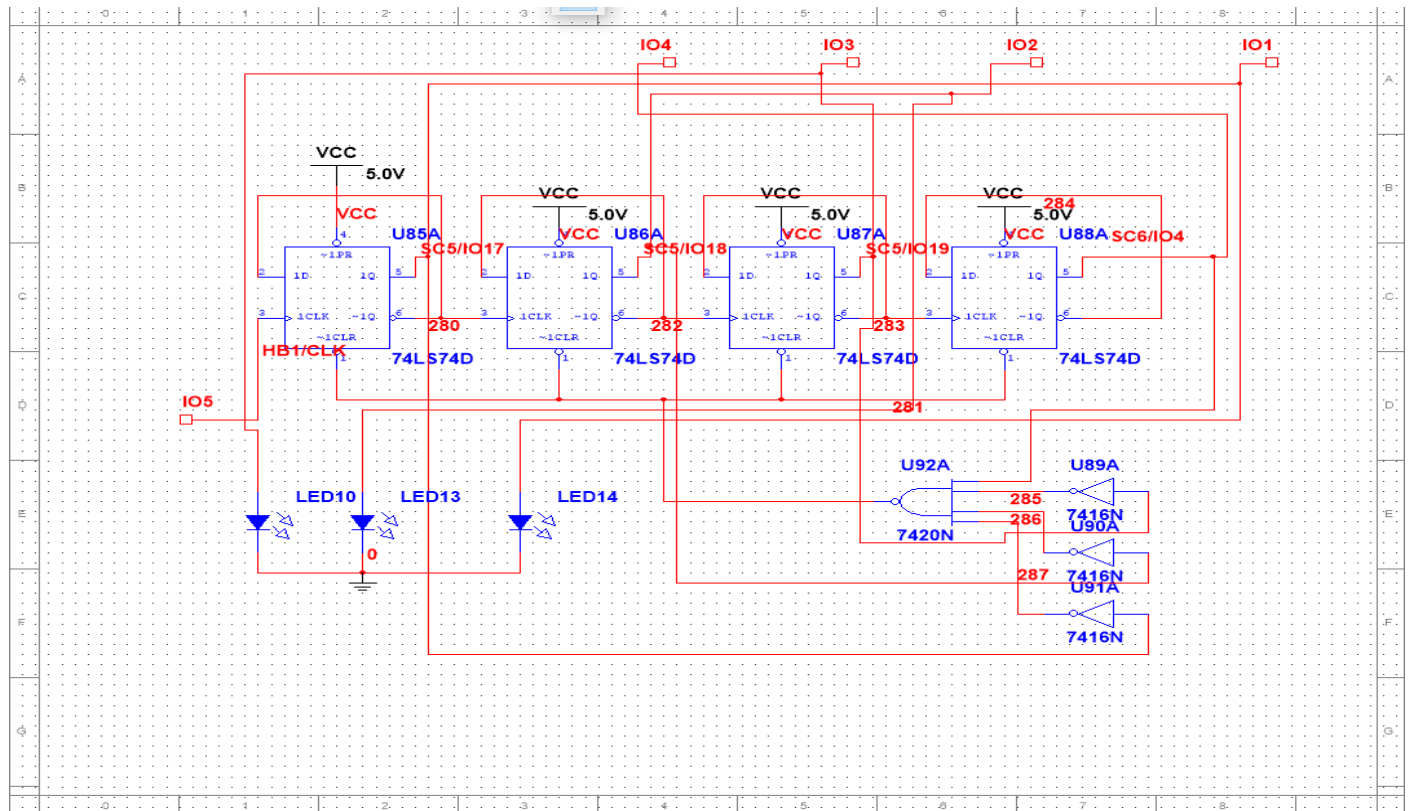


Sequential Timer Circuit: -

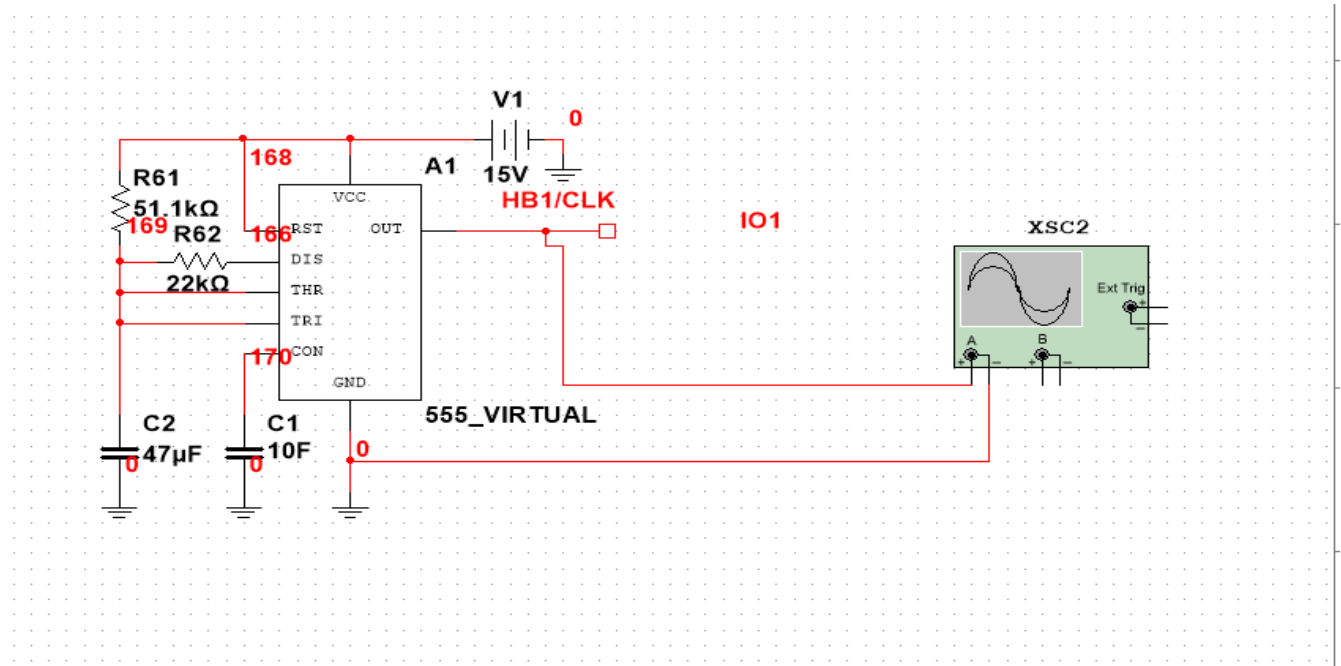


Delay Circuit: -

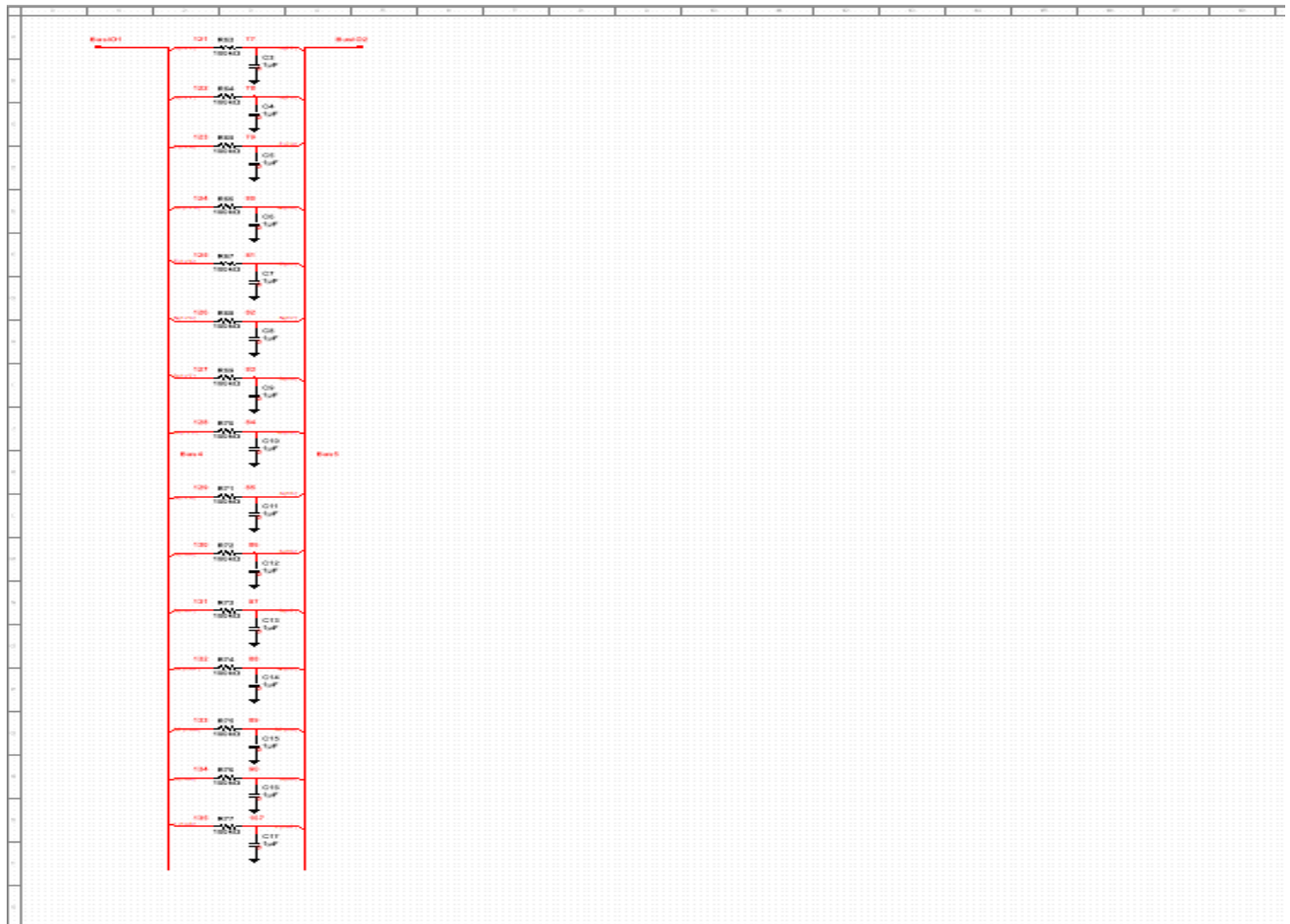

D-Flipflop Circuit: -

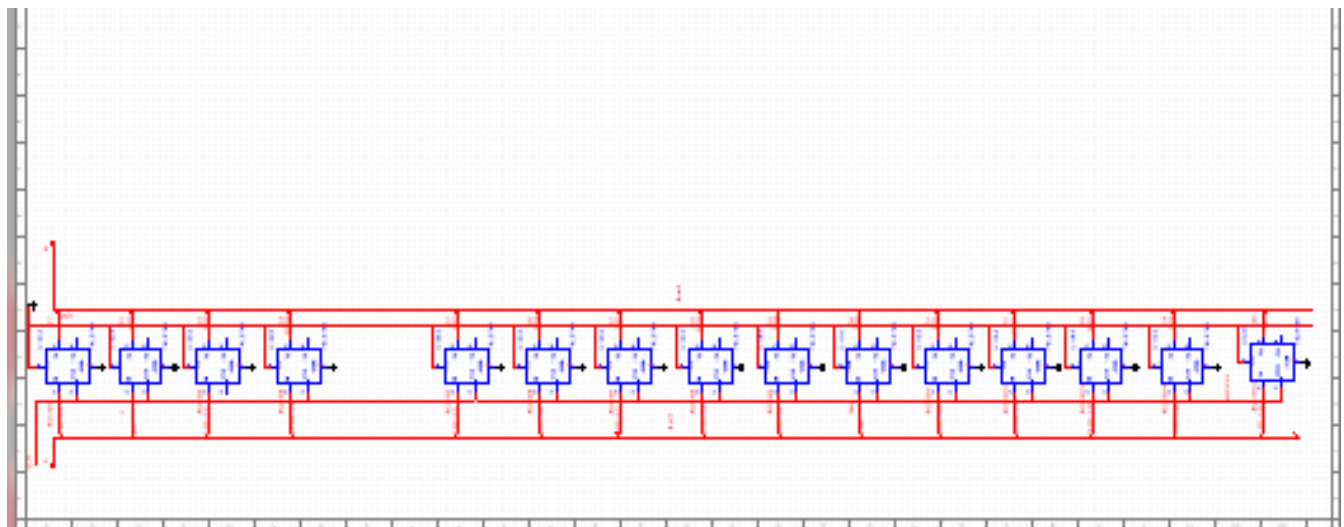

Shifttimer Circuit: -

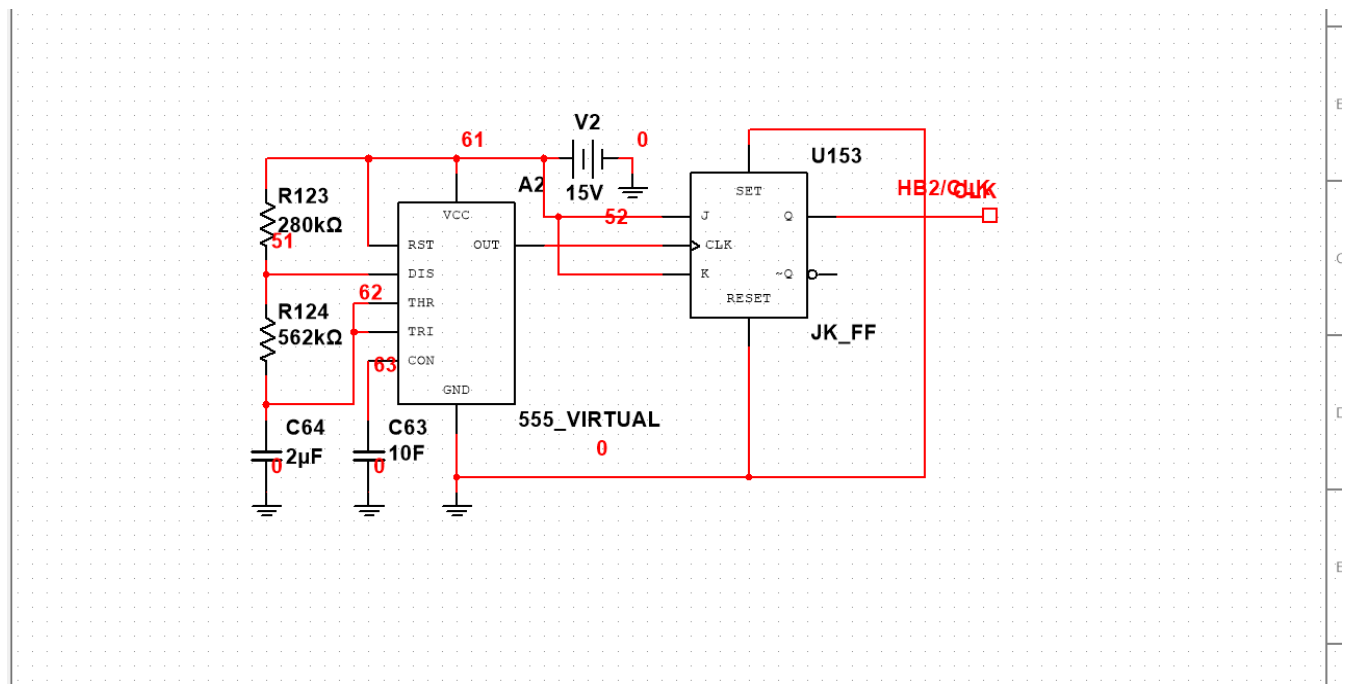

Team members:

- Kartik Udupa (IMT2018510)
- Rutvi (IMT2018519)
- Keshav (IMT2018511)
- Sriram G (IMT2018526)
- Sriman Reddy (IMT2018525)

